

I'm not a bot



























[illegible]

below figure. By voltage divider rule,  $V_{TH} = 200 \frac{j6}{4 + j6} = 200 \frac{690}{7.2156.3} = 200 \cdot 0.82533.7$   $V_{TH} = 16.533.7$  V By shorting the voltage source, we calculate the Thevenins equivalent impedance of the circuit as shown in figure. Therefore,  $Z_{TH} = \frac{(4 \cdot j6)}{4 + j6} = \frac{(4 \cdot 690)}{(7.2156.3)} = 3.3333.7$  Or  $2.77 + j1.85$  Ohms Hence, the Thevenins equivalent circuit across the load terminals is shown in below. Therefore to transfer the maximum power to the load, the value of the load impedance should be  $Z_L = Z_{TH} = 2.77 + j1.85$  ohms The maximum power delivered,  $P_{MAX} = \frac{V_{TH}^2}{4 \cdot R_{TH}} = \frac{(16.5)^2}{4(2.77)} = 272.25 / 11.08 = 24.5$  W Practical Application of Maximum Power Transfer Theorem Consider the practical example of a speaker with an impedance of 8 ohms. It is driven by an audio amplifier with an internal impedance of 500 ohms. The Thevenins equivalent circuit is also shown in figure. According to the maximum power transfer theorem, the power is maximized at the load if the load impedance is 500 ohms (same as internal impedance). Or else internal resistance has to be changed to 8 ohms to achieve the Maximum Power Transfer condition. However, it is not possible to change either of them. So, it is an impedance mismatch condition and it can be overcome by using an impedance matching transformer with its impedance transformation ratio of 500:8.

**Maximum power transfer theorem advantages and disadvantages. What is maximum power transfer theorem. Limitations of maximum power transfer theorem. Maximum power transfer theorem examples.**